

ESP32 Smart Medicine Reminder and Automatic Pill Dispensing System

Schematic Wiring Connections

Component	Pin	Connect To
ESP32	GPIO21	OLED SDA, DS1307 SDA
ESP32	GPIO22	OLED SCL, DS1307 SCL
ESP32	GPIO18	Servo PWM
ESP32	GPIO25	Buzzer +
ESP32	GPIO26	220Ω Resistor -> Red LED Anode
ESP32	GPIO27	220Ω Resistor -> Green LED Anode
ESP32	GPIO19	Push Button Terminal 1
ESP32	GND	RTC GND, OLED GND, Servo GND, Buzzer -, LED Cathodes, I
ESP32	5V	RTC VCC, Servo V+
ESP32	3.3V	OLED VCC

Notes

1. DS1307 and OLED share the I2C bus (GPIO21 SDA, GPIO22 SCL).
2. Push button uses INPUT_PULLUP in software. Connect one side to GPIO19 and the opposite side to GND.
3. Red and Green LEDs each require a 220Ω series resistor.
4. Servo is powered from the ESP32 5V pin in the Wokwi simulation.